

Choose  $V_{E1}$  so that  $\frac{V_{CC}}{10} < V_{E1} < \frac{V_{CC}}{3}$   
 $(V_{CC} = 18V)$

$$1.8V < V_{E1} < 6V$$

Choose  $V_{E1} = 4.2V$

### **$V_{E1}$ and $V_{C1}$ output voltage swing**

Make  $V_{C1}$  halfway between  $V_{E1}$  and  $V_{CC}$

$$V_{C1} = V_{E1} + (V_{CC} - V_{E1})/2$$

$$V_{C1} = 4.2 + (18 - 4.2)/2 = 11.1V$$

$$V_{CE1} = V_{RC1} = 6.9V$$

Swing is up to 7.5V approx

$$V_{E1} = V_{C1} - V_{BE2}$$

$$V_{E2} \approx V_{C1} - t = 11.1 - t =$$

$$V_{E2} \approx V_{C1} - 0.100 = 11.1 - 0.100 = 11V$$

### **Setting up $R_{E1}, R_{E2}$ and $R_{C1}$**

Set  $R_{E2}$  from  $V_{E2}$  and bias current  $R_{E2} = V_{E2}/I_{CQ2} = 11/15mA = 733\Omega$

Set  $R_{E1}$  from  $V_{E1}$  and bias current  $R_{E1} = V_{E2}/I_{CQ1} = 4.2/800\mu A = 5250\Omega$

Set  $R_{C1}$  from  $V_{E1}$  and bias current  $R_{C1} = V_{RC1}/I_{CQ1} = 6.9/800\mu A = 8625\Omega$

## Finding maximum Q1 base bias current

$$I_{B1max} = \frac{I_{CQ1}}{B_{min}}$$

$B_{min}$  from datasheet is 200

$$I_{B1max} = 800\mu A / 200 = 4\mu A$$

## Calculating R1 & R2

$$I_1 = 40\mu A, V_{B1} = 4.2 + 0.08 = 4.28V$$

Set  $R_1$  from  $V_{B1}$  and  $I_1$

$$R_1 = (V_{CC} - V_{B1}) / I_1 = (18 - 4.28) / 40\mu A = 343k\Omega$$

Set  $R_2$  from  $V_{B1}$  and  $I_1$

$$R_2 = V_{B1} / I_1 = 4.28 / 40\mu A = 107k\Omega$$

## C<sub>c</sub> and C<sub>E</sub> for cut-off frequencies

$$\frac{1}{2\pi f R_C}$$

$$\frac{1}{2\pi \times 18000 \times 11500} = 0.7n$$

### **C<sub>c</sub> and C<sub>E</sub> for cut-off frequency**

$$C_E = \frac{1}{2\pi f r_e}$$

$$r_e \approx \frac{25}{I_E}$$

$$r_{e1} \approx 25/0.5 = 50\Omega$$

$$C_E = 1/(2\pi * 60 * 50) = 50n$$

### **C<sub>1</sub> Input coupling capacitor**

$$\frac{1}{2\pi f r_{in}}$$

$$r_{be} + R_{E1} = B_{mn} R_{e1} + R_{E1} = 200 * 50 * 7000 = 17k\Omega$$

For 60Hz cut - off with this resistance (1/(2\pi \* 60 \* 17k)) C<sub>1</sub> = 0.03uF

We need the output resistance value  $r_{out} = \left( \frac{r_{be} + R_s}{b+1} \right)$

$$r_{be2} = b_{mn} r_{e2} = 200 * (25/18) = 280\Omega$$

$$R_s = R_c = 11500\Omega$$

$B_{max} = 450$  (we get this from the data sheet)

$$r_{out} = (280 + 11500)/450 = 26[700 = 26\Omega]$$

We need  $X_{C2} << r_{out}$  at lower cut off frequency so we do

$$C_2 >> \frac{1}{2\pi f r_{in}}$$

for 60Hz cut off =  $(1/2\pi * 60 * 26)$

$$C_2 = 10\mu F e$$

$$R_E = 5250\Omega$$

$$r_e \approx \frac{25}{I_e}$$

$$r_e \approx \frac{25}{0.5} = 50\Omega \text{ with } I_e \text{ in mV}$$

$$B = 200$$

$$RE = 5250 + 50 = 5300\Omega$$

$$5250.05(200 + 1) = 1065300$$

$$\frac{1}{s(CE)}+r_e$$

$$\frac{1}{2^*\pi^*1000(50n)}+\;50$$

$$s=jw=2\,\ast\,\pi\,\ast\,1000Hz$$