
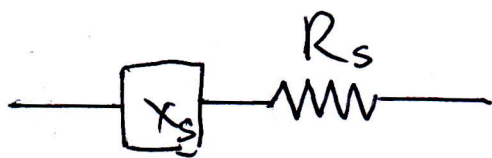


CONVERTING BETWEEN SERIES AND PARALLEL

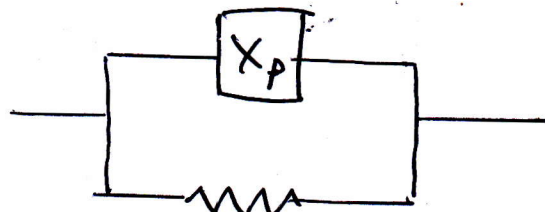

$$Q = \frac{X_s}{R_s}$$



$$Q = \frac{R_p}{X_p}$$

THESE NETWORKS LOOK IDENTICAL TO THE OUTSIDE WORLD.

$$R_s = \frac{R_p}{Q^2 + 1}$$

$$X_s = Q R_s$$

$$R_p = R_s (Q^2 + 1)$$


$$X_p = \frac{R_s}{Q}$$

IN MOST CASES WE CAN USE Q^2 AS AN APPROXIMATION FOR $Q^2 + 1$.

THE TWO NETWORKS HAVE THE SAME Q AND PHASE ANGLE.

①


2/2

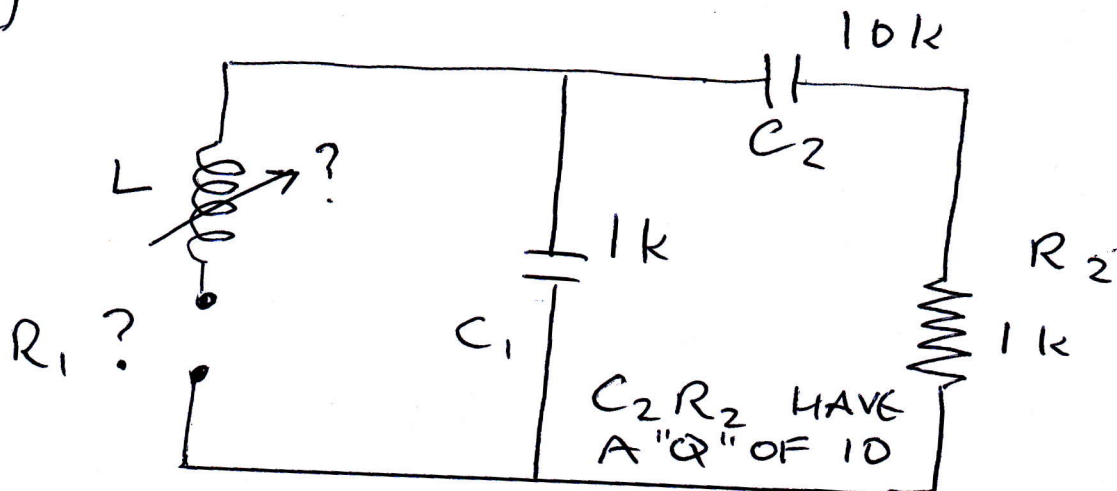

THE NECESSARY INDUCTANCE IS NOT INITIALLY KNOWN. IT HAS TO BE ADJUSTED TO OBTAIN RESONANCE.

CONVERT C_2 AND R_2 INTO A PARALLEL COMBINATION.

②

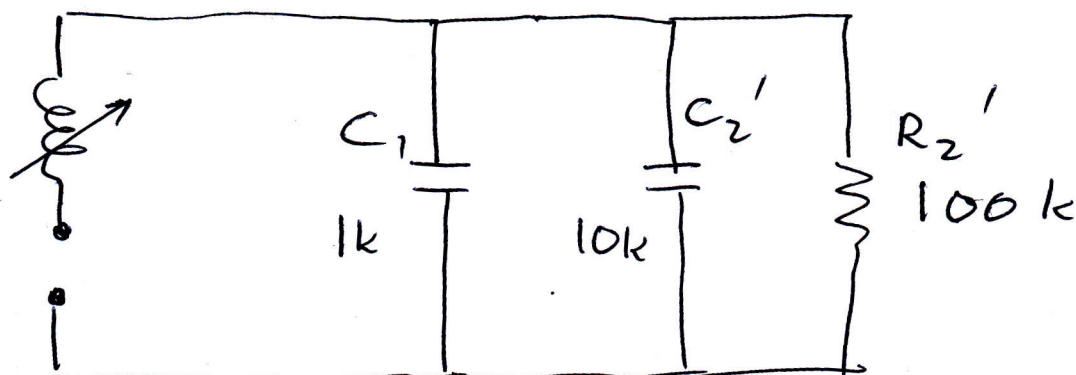

C_1 AND C_2' ADDED.

$C_2' R_2'$ HAVE A Q OF 10.

③

