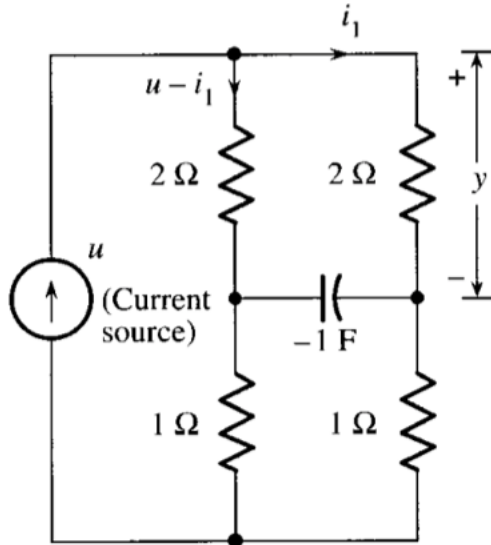


### Question 2:

Consider the below system where input is current source. The output  $y$  is the voltage across the 2-ohm resistor. Find the transfer function of the system and whether the given system is stable or not? Give Reasons for your answer?



### Question 3:

Consider the networks shown in fig (a). The transfer function from  $u_1$  to  $y_1$  of network  $M_1$  is  $G_1(s) = s/(s+1)$ . The transfer function from  $u_2$  to  $y_2$  of network  $M_2$  is  $G_2(s) = 2/(2+3s)$ . Now we connect them together i.e;  $y_1 = u_2$  fig(b)

Answer the following questions?

- Compute the transfer function from  $u_1$  to  $y_2$
- Determine the Natural Frequency
- Determine the Damping ratio
- Write the MATLAB CODE for the above-mentioned questions

